

Name :- Pritam Patel

Roll No:- 1901145

## EC362 VLSI Design

**Objective:-**Design of 12×12-bit Baugh Wooley Array Multiplier.

### **Theory:-**

**Array Multiplier:-**An array multiplier is a digital combinational circuit used for multiplying two binary numbers by employing an array of full adders and half adders. This array is used for the nearly simultaneous addition of the various product terms involved. For the product terms, an array of AND gates is used before the Adder array.

**Baugh Wooley Array Multiplier:-**In signed multiplication the length of the partial products and the number of partial products will be very high. The BaughWooley algorithm was introduced for signed multiplication. The Baugh-Wooley multiplication is one amongst the cost-effective ways to handle the sign bits. This method has been developed so as to style regular multipliers, suited to 2's complement numbers.

### **Baugh-Wooley Algorithm:-**

Let two n-bit numbers, number (X) and number (Y), X and Y can be written as:-

$$X = -x_{n-1}2^{n-1} + \sum_{i=0}^{n-2} x_i 2^i$$

$$Y = -y_{n-1}2^{n-1} + \sum_{i=0}^{n-2} y_i 2^i$$

Where  $x_{n-1}$  and  $y_{n-1}$  are the sign bits.

The product,  $P = X \times Y$ , is

$$P = \left[ (-x_{n-1}2^{n-1} + \sum_{i=0}^{n-2} x_i 2^i) \times (-y_{n-1}2^{n-1} + \sum_{i=0}^{n-2} y_i 2^i) \right]$$

$$=x_{n-1}y_{n-1}2^{2n-2} + \sum_{i=0}^{n-1} x_i 2^i \sum_{j=0}^{n-2} y_j 2^j - 2^{n-1} \sum_{i=0}^{n-2} x_i y_{n-1} 2^i - 2^{n-1} \sum_{j=0}^{n-2} x_{n-1} y_j 2^j$$

The first two terms of the above equation are positive and the last two terms are negative. In order to calculate the product, instead of subtracting the last two terms, it is possible to add the opposite values. The above equation signifies the Baugh-Wooley algorithm for the multiplication process in two's complement form.

### **Multiplication example of baugh-wooley algorithm:-**

•Let's consider 4 bit signed operands X and Y and 8 bit product P:-

$$X \Leftrightarrow (X_3, X_2, X_1, X_0), Y \Leftrightarrow (Y_3, Y_2, Y_1, Y_0), P \Leftrightarrow (P_7, P_6, P_5, P_4, P_3, P_2, P_1, P_0)$$

These are in the numerical form, we can calculate their numerical value :-

$$X = -x_3 2^3 + \sum_{i=0}^2 x_i 2^i \quad Y = -y_3 2^3 + \sum_{j=0}^2 y_j 2^j \quad P = -p_7 2^7 + \sum_{i=0}^6 p_i 2^i$$

$$P = (-x_3 2^3 + \sum_{i=0}^2 x_i 2^i)(-y_3 2^3 + \sum_{j=0}^2 y_j 2^j)$$

$$= x_3 y_3 2^6 + \sum_{i=0}^2 \sum_{j=0}^2 x_i y_j 2^{i+j} - \sum_{i=0}^2 x_i y_3 2^{i+3} - \sum_{j=0}^2 x_3 y_j 2^{j+3}$$

					X3	X2	X1	X0
					Y3	Y2	Y1	Y0
					X3Y0	X2Y0	X1Y0	X0Y0
				X3Y1	X2Y1	X1Y1	X0Y1	
		X3Y2	X2Y2	X1Y2	X0Y2			
1	X3Y3	X2Y3	X1Y3	X0Y3				
P7	P6	P5	P4	P3	P2	P1	P0	

### Baugh wooley multiplier architecture for 4×4 bit:-

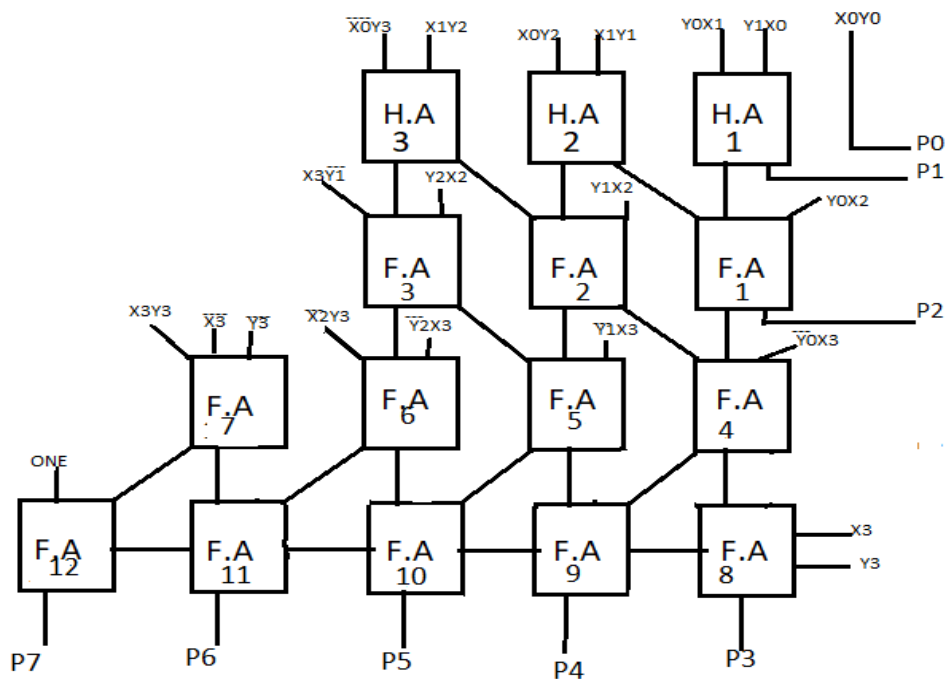



Fig 1:-BW architecture for 4 bit

### Multiplication of 12×12 signed bit:-

Let's consider 12 bit signed operands X and Y and 24 bit product P:-

$$P_4, P_3, P_2, P_1, P_0)$$

## Baugh wooley multiplier architecture for 12×12 bit:-

 


**Fig2 :-BW architecture for 12×12 bit**

Output Waveform For Some Random Number Taken In Test Bench:-



**Fig 4:-Output waveform in binary**


## Schematic of 12x12 Bit Baugh-Wooley Multiplier:-

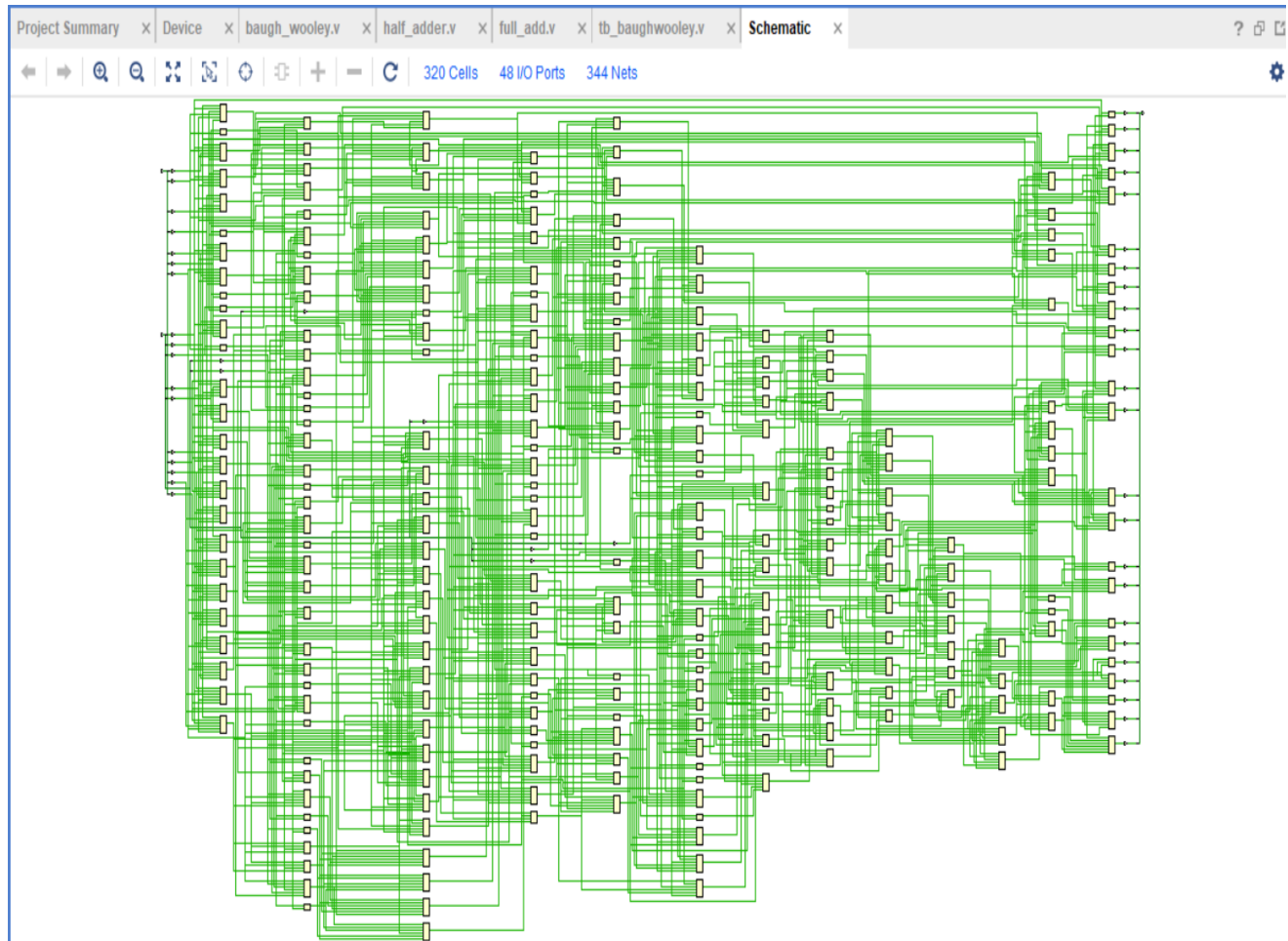

**Fig 5:-Schematic for 12x12 bit BW multiplier**

## Hardware Result:-

### Device:-

 

### Hardware implementation:-

+-----+-----+-----+-----+-----+				
	Total On-Chip Power (W)		25.875	
	Design Power Budget (W)		Unspecified*	
	Power Budget Margin (W)		NA	
	Dynamic (W)		25.644	
	Device Static (W)		0.231	
	Effective TJA (C/W)		1.9	
	Max Ambient (C)		36.3	
	Junction Temperature (C)		73.7	
	Confidence Level		Low	
	Setting File		---	
	Simulation Activity File		---	
	Design Nets Matched		NA	
+-----+-----+-----+-----+-----+				
+-----+-----+-----+-----+-----+				
	On-Chip		Power (W)	
	Used		Available	
	Utilization (%)			
+-----+-----+-----+-----+-----+				
	Slice Logic		3.085	
	LUT as Logic		260	
	Signals		41000	
	I/O		191	
	Static Power		284	
	Total		300	
			16.00	
+-----+-----+-----+-----+-----+				



## **Conclusion:-**

Baugh Wooley multiplier exhibits less delay, low power dissipation and the area occupied is also small compared to other array multipliers.

## **CODE:-**

### **DESIGN MODULE**

**// half adder component used in the multiplier**

```
module half_adder(a, b, s, cout);
```

```
input a, b;
```

```
output s, cout;
```

```
assign s = a^b;
```

```
assign cout = a&b;
```

```
endmodule
```

**// full adder component used in the multiplier**

```
module full_add(a, b, cin, s, cout);
```

```
input a, b, cin;
```

```
output s, cout;
```

```
assign s = a^b^cin;
```

```
assign cout = (a&b) | (b&cin) | (a&cin);
```

```
endmodule
```

**// 12-bit by 12-bit Baugh-Wooley signed multiplier**

```
module baugh_wooley(x, y, p);
```

```
input [11:0] x, y;
```

```
output [23:0] p;
```

```

// constant logic-one value
supply1 one;

// Internal results which is given to next stage adders
wire t1, t2, t3, t4, t5, t6, t7, t8, t9, t10, t11, t12, t13, t14, t15, t16, t17, t18, t19, t20, t21, t22, t23,
t24, t25, t26, t27, t28, t29, t30, t31, t32, t33, t34, t35, t36, t37, t38, t39, t40, t41, t42, t43, t44, t45, t46, t47, t48,
T49, t50, t51, t52, t53, t54, t55, t56, t57, t58, t59, t60, t61, t62, t63, t64, t65, t66, t67, t68, t69, t70, t71, t72, t73,
t74, t75, t76, t77, t78, t79, t80, t81, t82, t83, t84, t85, t86, t87, t88, t89, t90, t91, t92, t93, t94, t95, t96, t97, t98,
t99, t100, t101, t102, t103, t104, t105, t106, t107, t108, t109, t110, t111, t112, t113, t114, t115, t116, t117,
t118, t119, t120, t121, t122, t123, t124, t125, t126, t127, t128, t129, t130, t131, t132, t133, t134, t135, t136,
t137, t138, t139, t140, t141, t142, t143, t144, t145, t146, t147, t148, t149, t150, t151, t152, t153, t154, t155,
t156, t157, t158, t159, t160, t161, t162, t163, t164, t165, t166, t167, t168, t169, t170, t171, t172, t173, t174,
t175, t176, t177, t178, t179, t180, t181, t182, t183, t184, t185, t186, t187, t188, t189, t190, t191, t192
, t193, t194, t195, t196, t197, t198, t199, t200, t201, t202, t203, t204, t205, t206, t207, t208, t209, t210, t211,
t212, t213, t214, t215, t216, t217, t218, t219, t220, t221, t222, t223, t224, t225, t226, t227, t228, t229,
t230, t231, t232, t233, t234, t235, t236, t237, t238, t239, t240, t241, t242, t243, t244, t245, t246, t247;

// structural description of the multiplier circuit
assign p[0] = x[0]&y[0];

half_adder ha1(x[1]&y[0], x[0]&y[1], p[1], t1);
half_adder ha2(x[2]&y[0], x[1]&y[1], t2, t3);
half_adder ha3(x[3]&y[0], x[2]&y[1], t4, t5);
half_adder ha4(x[4]&y[0], x[3]&y[1], t6, t7);
half_adder ha5(x[5]&y[0], x[4]&y[1], t8, t9);
half_adder ha6(x[6]&y[0], x[5]&y[1], t10, t11);
half_adder ha7(x[7]&y[0], x[6]&y[1], t12, t13);
half_adder ha8(x[8]&y[0], x[7]&y[1], t14, t15);
half_adder ha9(x[9]&y[0], x[8]&y[1], t16, t17);
half_adder ha10(x[10]&y[0], x[9]&y[1], t18, t19);
half_adder ha11(x[11]&~y[0], x[10]&y[1], t20, t21);

```

```
full_add fa1(t2, t1, x[0]&y[2], p[2], t22);
full_add fa2(t4, t3, x[1]&y[2], t23, t24);
full_add fa3( t6,t5, x[2]&y[2], t25, t26);
full_add fa4( t8, t7,x[3]&y[2], t27, t28);
full_add fa5( t10,t9,x[4]&y[2], t29, t30);
full_add fa6(t12,t11,x[5]&y[2], t31, t32);
full_add fa7(t14,t13,x[6]&y[2], t33,t34);
full_add fa8(t16,t15,x[7]&y[2], t35, t36);
full_add fa9(t18,t17,x[8]&y[2], t37, t38);
full_add fa10(t20,t19,x[9]&y[2], t39, t40);
full_add fa11(t21,x[11]&~y[1],x[10]&y[2],t41,t42);
```

```
full_add fa12(t23,t22, x[0]&y[3], p[3], t43);
full_add fa13(t25,t24, x[1]&y[3], t44, t45);
full_add fa14(t27,t26, x[2]&y[3], t46, t47);
full_add fa15(t29,t28, x[3]&y[3], t48, t49);
full_add fa16(t31,t30,x[4]&y[3], t50, t51);
full_add fa17(t33,t32,x[5]&y[3], t52, t53);
full_add fa18(t35,t34,x[6]&y[3], t54,t55);
full_add fa19(t37,t36,x[7]&y[3], t56, t57);
full_add fa20(t39,t38,x[8]&y[3], t58, t59);
full_add fa21(t41,t40,x[9]&y[3], t60, t61);
full_add fa22(t42,x[11]&~y[2],x[10]&y[3],t62,t63);
```

```
full_add fa23( t44,t43, x[0]&y[4], p[4], t64);
full_add fa24( t46,t45, x[1]&y[4], t65, t66);
```

```
full_add fa25( t48,t47, x[2]&y[4], t67, t68);
full_add fa26( t50,t49, x[3]&y[4], t69, t70);
full_add fa27( t52,t51, x[4]&y[4], t71, t72);
full_add fa28(t54,t53, x[5]&y[4], t73, t74);
full_add fa29(t56,t55, x[6]&y[4], t75,t76);
full_add fa30(t58,t57,x[7]&y[4], t77, t78);
full_add fa31(t60,t59,x[8]&y[4], t79, t80);
full_add fa32(t62,t61,x[9]&y[4], t81, t82);
full_add fa33(t63,x[11]&~y[3],x[10]&y[4],t83,t84);
```

```
full_add fa34(t65,t64, x[0]&y[5], p[5], t85);
full_add fa35(t67,t66, x[1]&y[5], t86, t87);
full_add fa36(t69,t68, x[2]&y[5], t88, t89);
full_add fa37(t71,t70, x[3]&y[5], t90, t91);
full_add fa38(t73,t72,x[4]&y[5], t92, t93);
full_add fa39(t75,t74,x[5]&y[5], t94, t95);
full_add fa40(t77,t76,x[6]&y[5], t96,t97);
full_add fa41(t79,t78,x[7]&y[5], t98, t99);
full_add fa42(t81,t80,x[8]&y[5], t100, t101);
full_add fa43(t83,t82,x[9]&y[5], t102, t103);
full_add fa44(t84,x[11]&~y[4],x[10]&y[5],t104,t105);
```

```
full_add fa45( t86,t85, x[0]&y[6], p[6], t106);
full_add fa46( t88,t87, x[1]&y[6], t107, t108);
full_add fa47( t90,t89, x[2]&y[6], t109, t110);
full_add fa48( t92,t91, x[3]&y[6], t111, t112);
full_add fa49( t94,t93,x[4]&y[6], t113, t114);
full_add fa50(t96,t95,x[5]&y[6], t115, t116);
```

```
full_add fa51(t98,t97,x[6]&y[6], t117,t118);
full_add fa52(t100,t99,x[7]&y[6], t119, t120);
full_add fa53(t102,t101,x[8]&y[6], t121, t122);
full_add fa54(t104,t103,x[9]&y[6], t123, t124);
full_add fa55(t105,x[11]&~y[5],x[10]&y[6],t125,t126);
```

```
full_add fa56(t107,t106, x[0]&y[7], p[7], t127);
full_add fa57(t109,t108, x[1]&y[7], t128, t129);
full_add fa58( t111,t110, x[2]&y[7], t130, t131);
full_add fa59( t113,t112, x[3]&y[7], t132, t133);
full_add fa60( t115,t114,x[4]&y[7], t134, t135);
full_add fa61(t117,t116,x[5]&y[7], t136, t137);
full_add fa62(t119,t118,x[6]&y[7], t138,t139);
full_add fa63(t121,t120,x[7]&y[7], t140, t141);
full_add fa64(t123,t122,x[8]&y[7], t142, t143);
full_add fa65(t125,t124,x[9]&y[7], t144, t145);
full_add fa66(t126,x[11]&~y[6],x[10]&y[7],t146,t147);
```

```
full_add fa67(t128,t127, x[0]&y[8], p[8], t148);
full_add fa68( t130,t129, x[1]&y[8], t149, t150);
full_add fa69( t132,t131, x[2]&y[8], t151, t152);
full_add fa70( t134,t133, x[3]&y[8], t153, t154);
full_add fa71( t136,t135,x[4]&y[8], t155, t156);
full_add fa72(t138,t137,x[5]&y[8], t157, t158);
full_add fa73(t140,t139,x[6]&y[8], t159,t160);
full_add fa74(t142,t141,x[7]&y[8], t161, t162);
full_add fa75(t144,t143,x[8]&y[8], t163, t164);
full_add fa76(t146,t145,x[9]&y[8], t165, t166);
```

full\_add fa77(t147,x[11]&~y[7],x[10]&y[8],t167,t168);

full\_add fa78( t149,t148, x[0]&y[9], p[9], t169);

full\_add fa79( t151,t150, x[1]&y[9], t170, t171);

full\_add fa80( t153,t152, x[2]&y[9], t172, t173);

full\_add fa81( t155,t154, x[3]&y[9], t174, t175);

full\_add fa82( t157,t156,x[4]&y[9], t176, t177);

full\_add fa83(t159,t158,x[5]&y[9], t178, t179);

full\_add fa84(t161,t160,x[6]&y[9], t180,t181);

full\_add fa85(t163,t162,x[7]&y[9], t182, t183);

full\_add fa86(t165,t164,x[8]&y[9], t184, t185);

full\_add fa87(t167,t166,x[9]&y[9], t186, t187);

full\_add fa88(t168,x[11]&~y[8],x[10]&y[9],t188,t189);

full\_add fa89( t170,t169, x[0]&y[10], p[10], t190);

full\_add fa90( t172,t171, x[1]&y[10], t191, t192);

full\_add fa91( t174,t173, x[2]&y[10], t193, t194);

full\_add fa92( t176,t175, x[3]&y[10], t195, t196);

full\_add fa93( t178,t177,x[4]&y[10], t197, t198);

full\_add fa94(t180,t179,x[5]&y[10], t199, t200);

full\_add fa95(t182,t181,x[6]&y[10], t201,t202);

full\_add fa96(t184,t183,x[7]&y[10], t203, t204);

full\_add fa97(t186,t185,x[8]&y[10], t205, t206);

full\_add fa98(t188,t187,x[9]&y[10], t207, t208);

full\_add fa99(t189,x[11]&~y[9],x[10]&y[10],t209,t210);

full\_add fa100( t191,t190, ~x[0]&y[11], t211, t212);

```
full_add fa101( t193,t192, ~x[1]&y[11], t213, t214);
full_add fa102( t195,t194, ~x[2]&y[11], t215, t216);
full_add fa103( t197,t196, ~x[3]&y[11], t217, t218);
full_add fa104( t199,t198,~x[4]&y[11], t219, t220);
full_add fa105(t201,t200,~x[5]&y[11], t221, t222);
full_add fa106(t203,t202,~x[6]&y[11], t223,t224);
full_add fa107(t205,t204,~x[7]&y[11], t225, t226);
full_add fa108(t207,t206,~x[8]&y[11], t227, t228);
full_add fa109(t209,t208,~x[9]&y[11], t229, t230);
full_add fa110(t210,x[11]&~y[10],~x[10]&y[11],t231,t232);
full_add fa111(~x[11],~y[11],x[11]&y[11],t233, t234);
```

```
full_add fa112(t211, x[11],y[11], p[11], t235);
full_add fa113( t213,t212,t235, p[12], t236);
full_add fa114( t215,t214,t236 ,p[13], t237);
full_add fa115( t217,t216,t237 ,p[14], t238);
full_add fa116( t219,t218,t238, p[15], t239);
full_add fa117(t221,t220,t239, p[16], t240);
full_add fa118(t223,t222,t240,p[17],t241);
full_add fa119(t225,t224,t241,p[18], t242);
full_add fa120(t227,t226,t242,p[19], t243);
full_add fa121(t229,t228,t243,p[20], t244);
full_add fa122(t231,t230,t244,p[21],t245);
full_add fa123(t233,t232,t245,p[22],t246);
full_add fa124(1,t234,t246,p[23],t247);
```

```
endmodule
```

### TEST BENCH:-

```
module test;

wire signed [23:0] p;
reg signed [11:0] x,y;
baugh_wooley my_booth(.x(x),.y(y),.p(p));

initial

begin

$monitor($time,"      ",x," *",y," = ", p);

x = 12'b101000000000;
y = 12'b010000000000;
#10
x = 12'b110101001010;
y = 12'b101010101101;
#10
x = 12'b011100000000;
y = 12'b000000000000;
#10
x = 12'b1;
y = 12'b1;
#10
x = 12'b101111000000;
y = 12'b1101;
#10
x = 12'b101010100000;
y = 12'b100011000000;
#10
x = 12'b110001;
y = 12'b11100;
```



```
#10
```

```
x = 12'b1000;
```

```
y = 12'b10111111;
```

```
end
```

```
endmodule
```